

# Lab Report 5

Name: Vishak Kashyap K

Roll Number: 2023113012

## Group: 9

## **Experiment 5 (Part A) - SR Latch**

## Objective:


To design, assemble and test an SR Latch.

## Electronic Components Required:


1. Digital Test Kit
  2. CD4001 IC NOR Gate
  3. Voltage Supply
  4. Normal Wires

## Reference Circuit:

- ## 1. Tinkercad Screenshot

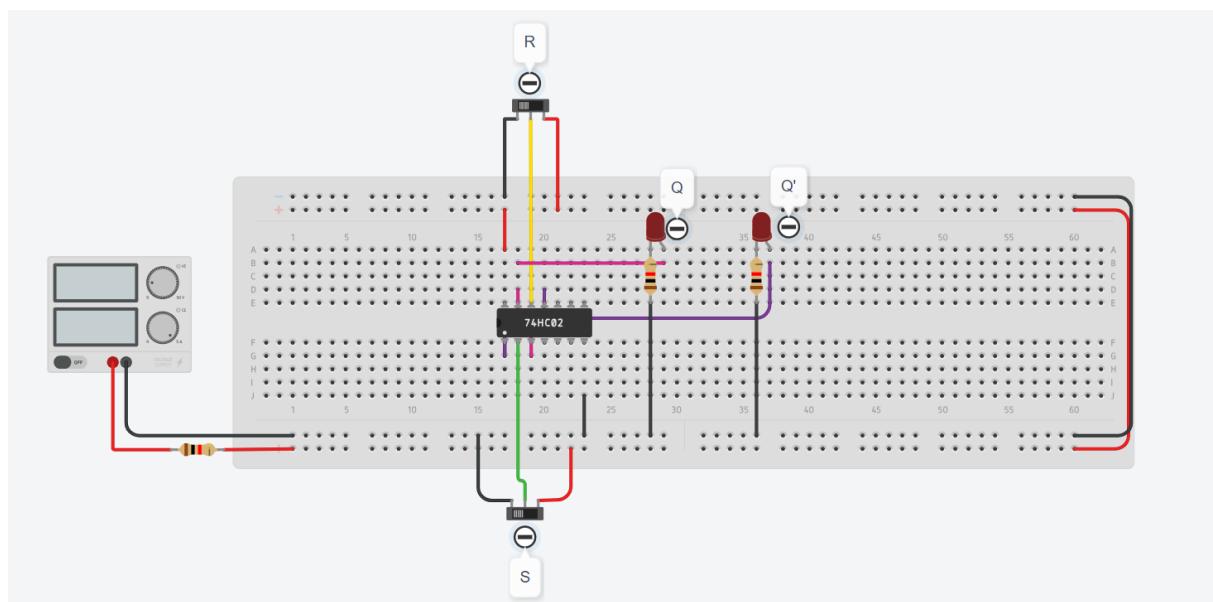


## 2. Circuit Diagram

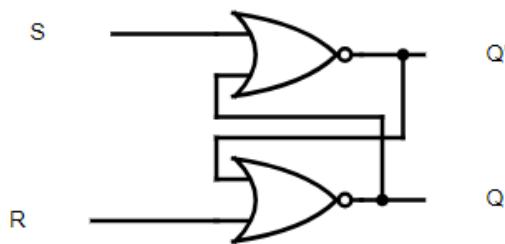


### Procedure:

1. Attach the CD4001 IC to the breadboard. Connect the VCC and GND pins of the breadboard to those of the ICs.
2. Using two switches as inputs for two NOR gates and the outputs of each as a second input for the other.
3. Connect the outputs to LEDs.
4. View the outputs for different values of input and tabulate the observations.

### Observations:

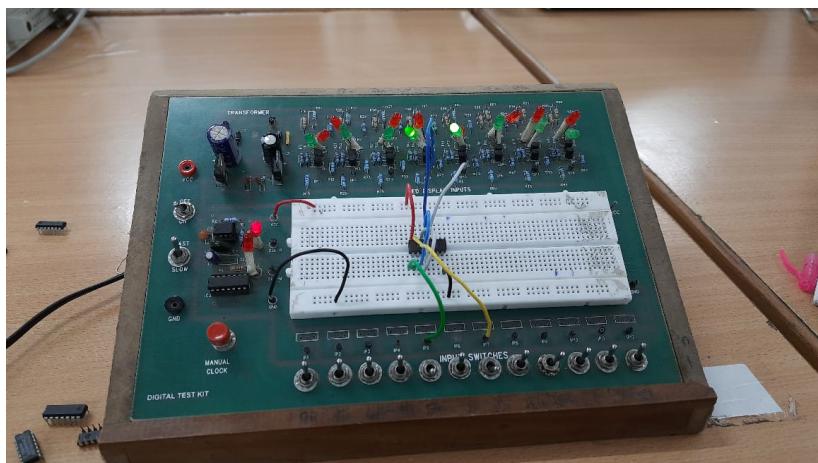

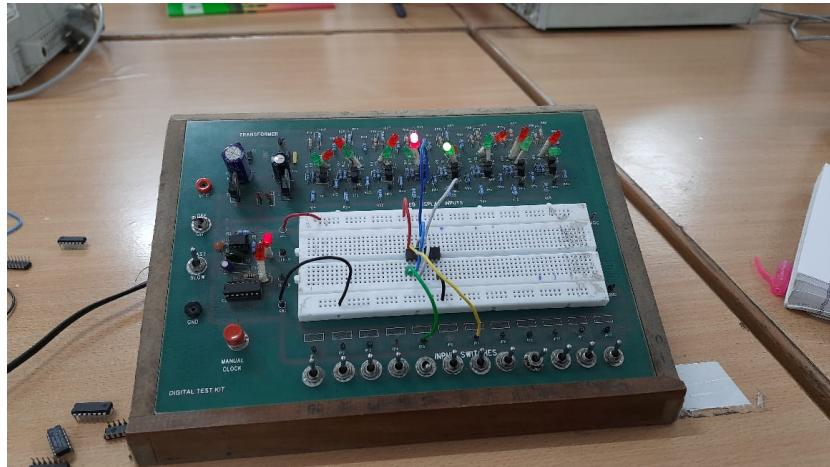

1. The expected working of the SR Latch is as follows:

S	R	Q	Q'
0	0		
0	1		
1	0		
1	1		

2. For the given inputs, we observe the following outputs.

<b>R</b>	<b>S</b>	<b>Q</b>	<b>Q'</b>
0	1	1	0
0	0	1	0
1	0	0	1
0	0	0	1
0	1	1	0
1	0	0	1
0	1	1	0
0	0	1	0
1	1	0 (Forbidden)	0 (Forbidden)
0	0	Random	
1	0	0	1
1	1	0 (Forbidden)	0 (Forbidden)
0	0	Random	
0	1	1	0
1	1	0 (Forbidden)	0 (Forbidden)
0	0	Random	

### Conclusions:

We have created an RS Latch, verified its working and observed its operation for a given set of inputs.

### Link for Tinkercad Simulation:

[https://www.tinkercad.com/things/3AYyZhgOgeI-5a-sr-latch-/editel?sharecode=1i9ETRpt9OGOupuk\\_gfb6A8RrgKj2YeraFIHqfymRkl](https://www.tinkercad.com/things/3AYyZhgOgeI-5a-sr-latch-/editel?sharecode=1i9ETRpt9OGOupuk_gfb6A8RrgKj2YeraFIHqfymRkl)

## Experiment 5 (Part B) - JK Master-Slave Flip-Flop

### **Objective:**


Designing, assembling and testing a JK Flip Flop.

### **Electronic Components Required:**


1. CD4012 IC NAND Gate
2. CD4001 IC NOR Gate
3. Normal Wires
4. Digital Test Kit
5. Voltage Supply

### **Reference Circuit:**

#### 1. Circuit Diagram

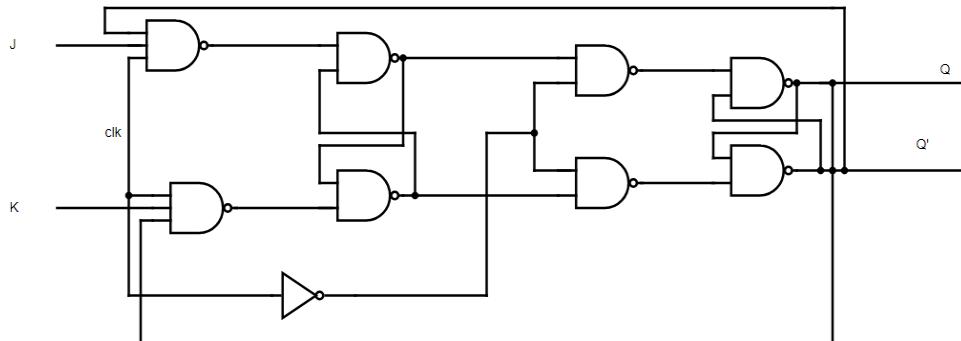



#### 2. Tinkercad Screenshot

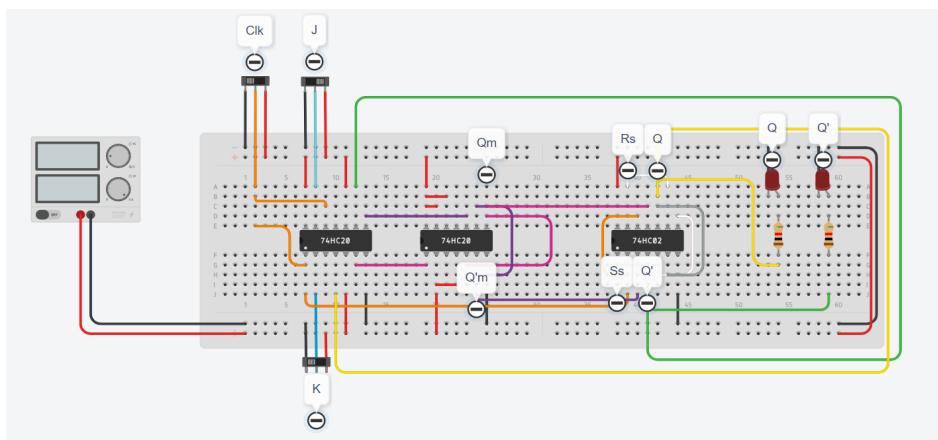

## **Procedure:**

1. Connect the CD4012 and CD4001 ICs to the breadboard. Connect the VCC and GND pins to those of the Breadboard.
2. Make all the connections to the ICs as per the reference diagram.
3. Observe the outputs of the Flip flop for various values of input. Verify its working and tabulate the outputs.

## **Observations:**

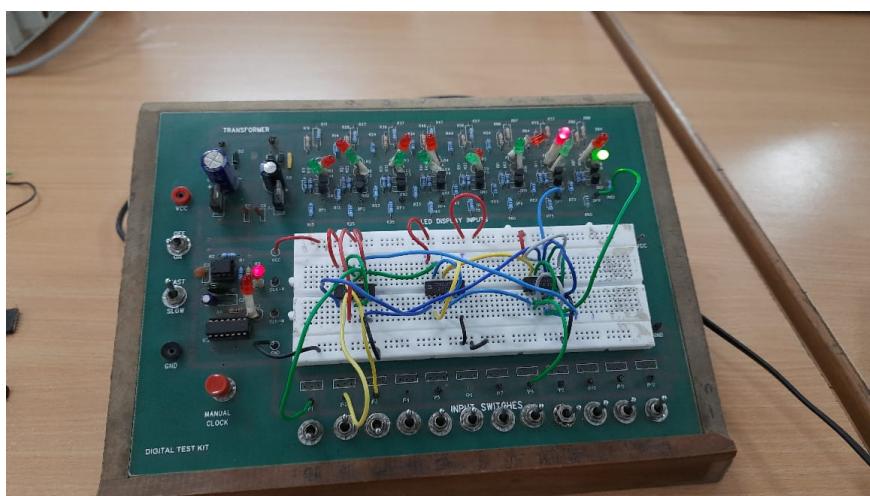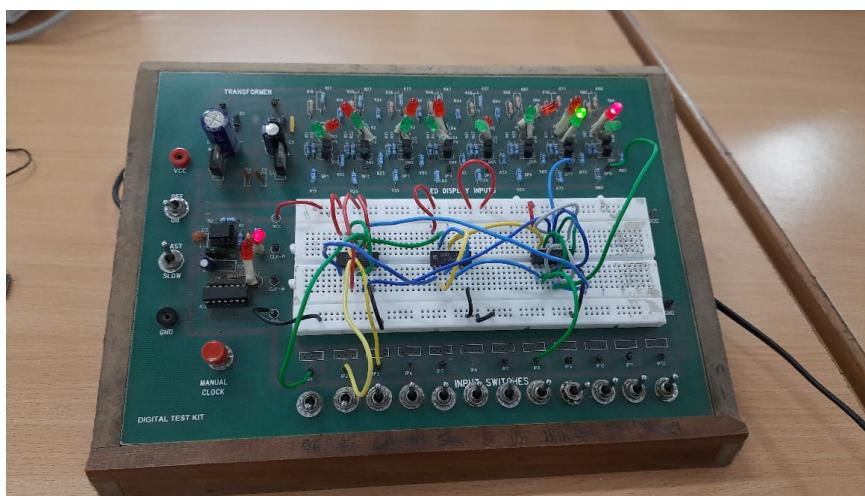

We obtain the following truth table:

J	K	Q(t+1)
0	0	Q(t) [Unchanged]
0	1	0 [Reset]
1	0	1 [Set]
1	1	Q'(t) [Complements]

### Conclusions:

We have created a JK Flip Flop and verified its working.

### Link for Tinkercad Simulation:

<https://www.tinkercad.com/things/IY8Xi6O6CUZ-5b-jk-master-slave-flip-flop/editel?sharecode=BeIXjz0Q8fh69ergIv1YuQ9vy7zBdgS2MVwP4BetHg0>

## Experiment 5 (Part C) - 4-Bit Up-Down Counter

### **Objective:**


To design a 4-bit Up-Down Counter that first goes UP from 0(0000) to 15(1111), then goes down from 15 to 0, then goes UP, and this cycle repeats until the simulation stops.

### **Electronic Components Required:**


1. Arduino UNO
2. Digital Test Kit
3. Normal Wires
4. Jumper Wires
5. Voltage Supply

### **Reference Circuit:**

1. Circuit Diagram

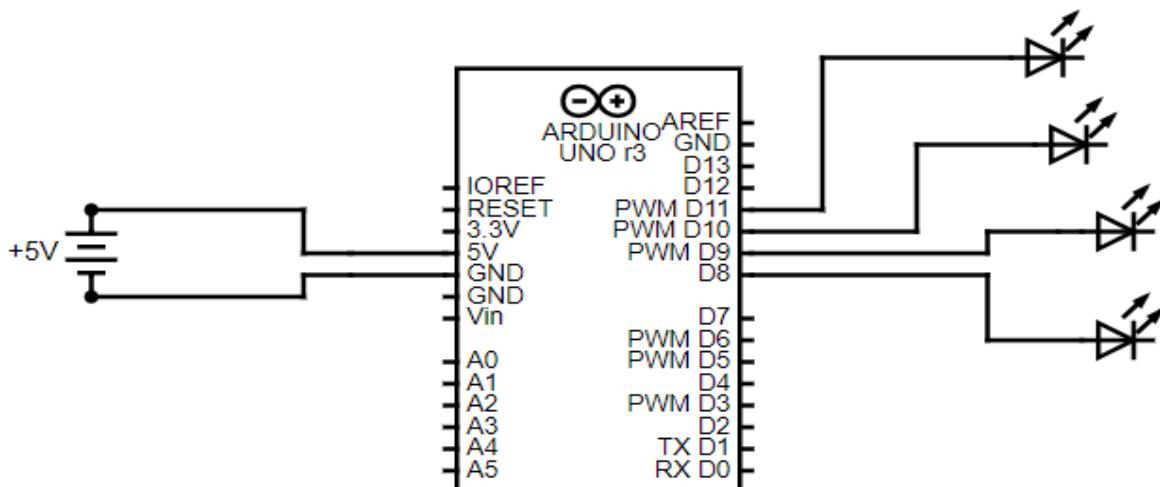


## 2. Tinkercad Screenshot

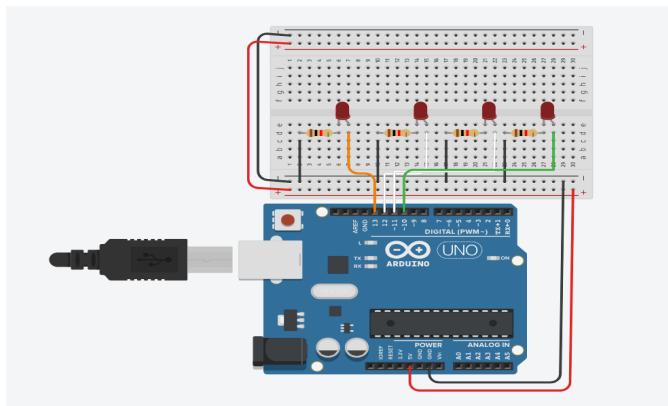

### Procedure:

1. Using the Timer library, implement a 4-bit counter. The bit outputs of the 4-bit ripple counter will be represented by LEDs. (On LED for each bit)
2. Initialise a Timer t and use the t.oscillate function to toggle the pin values in a pre-defined time period (each pin will have a different time period)
3. Once the ripple counter reaches 15(1111), make it go down to 0. Stop existing timers using t.stop.
4. Use t.every to fire a function after a set-interval of time that will do two tasks: stop all timers and restart them in the opposite direction.

### Observation:

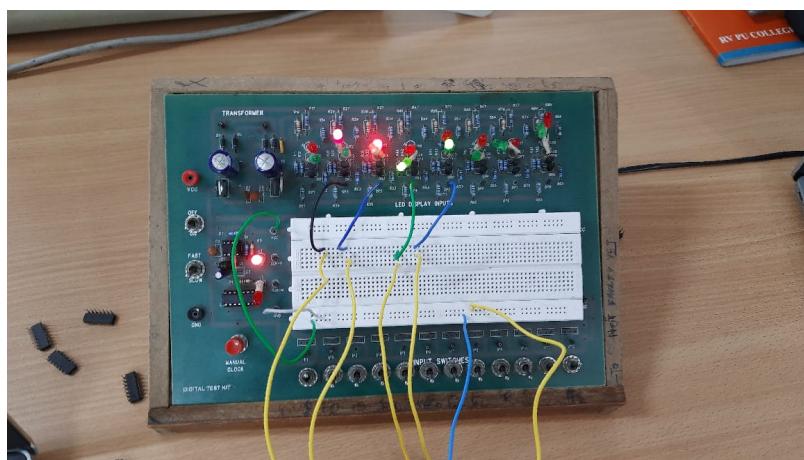

## Code:

```
Intro_to_Arduino_Workshop.ino
93  };
94  #endif
95
96 ///// YOUR CODE STARTS HERE
97
98 Timer t;
99 int pin0 = 3;
100 int pin1 = 6;
101 int pin2 = 9;
102 int pin3 = 13;
103
104 bool forward = true;
105 int t0,t1,t2,t3;
106 int d = 1000;
107
108 void setup()
109 {
110     Serial.begin(9600);
111     pinMode(pin0, OUTPUT);
112     pinMode(pin1, OUTPUT);
113     pinMode(pin2, OUTPUT);
114     pinMode(pin3, OUTPUT);
115     t0 = t.oscillate(pin0, d, LOW);
116     t1 = t.oscillate(pin1, d << 1, LOW);
117     t2 = t.oscillate(pin2, d << 2, LOW);
118     t3 = t.oscillate(pin3, d << 3, LOW);
119
120     t.every(d << 4, stopAllTimers);
121 }
122
123 // 1 unit of your timer = 500ms in real time
124
125 void loop() {
126     t.update();
```

```
125     void loop() {
126         t.update();
127     }
128
129     // "every" X milliseconds
130     void stopAllTimers()
131     {
132         t.stop(t0);
133         t.stop(t1);
134         t.stop(t2);
135         t.stop(t3);
136         forward = !forward;
137         if (forward)
138         {
139             t0 = t.oscillate(pin0, d, LOW);
140             t1 = t.oscillate(pin1, d << 1, LOW);
141             t2 = t.oscillate(pin2, d << 2, LOW);
142             t3 = t.oscillate(pin3, d << 3, LOW);
143         }
144         else
145         {
146             t0 = t.oscillate(pin0, d, HIGH);
147             t1 = t.oscillate(pin1, d << 1, HIGH);
148             t2 = t.oscillate(pin2, d << 2, HIGH);
149             t3 = t.oscillate(pin3, d << 3, HIGH);
150         }
151     }
152
153 ///// YOUR CODE ENDS HERE
154
155 // For Arduino 1.0 and earlier
156 // #if defined(ARDUINO) && ARDUINO >= 100
157 // #include "Arduino.h"
```

## **Conclusions:**

We have successfully created a 4 bit Up-Down Counter that first goes UP from 0(0000) to 15(1111), then goes down from 15 to 0, then goes UP , and this cycle repeats until the simulation stops.

## **Link for Tinkercad Simulation:**

<https://www.tinkercad.com/things/cmxmlvYNdGEq-5c-up-down-counter/edit?sharecode=9MDBIm3a5C2I6kvzuuWUzAbCoA-5kuxHecXMqexdB0>